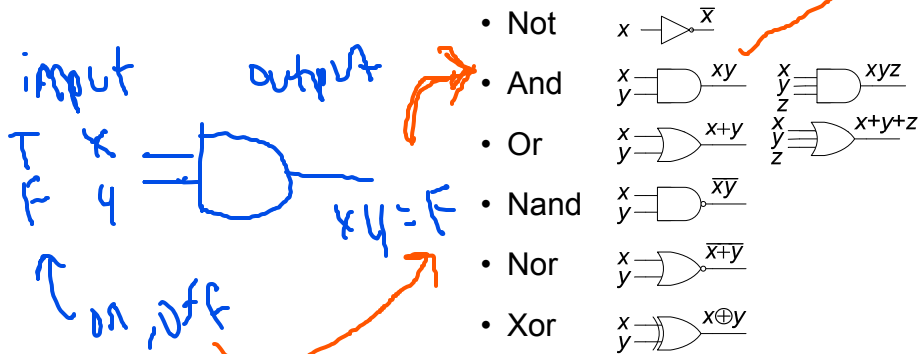




PROBLEM OF THE DAY 7c

Logic Gates and Circuits

(Material from <http://homepage.cs.uiowa.edu/~hzhang/c19/ch01c.pdf>)**1. Logic Gates:** Physical devices that perform Boolean operations are called *logic gates*.**2. Circuits:** Logic gates can be combined into a *circuit* to perform more complicated Boolean expressions.

Example: Build a circuit to perform the Boolean operation Xor using only And, Or, and Not logic gates.

Solution:

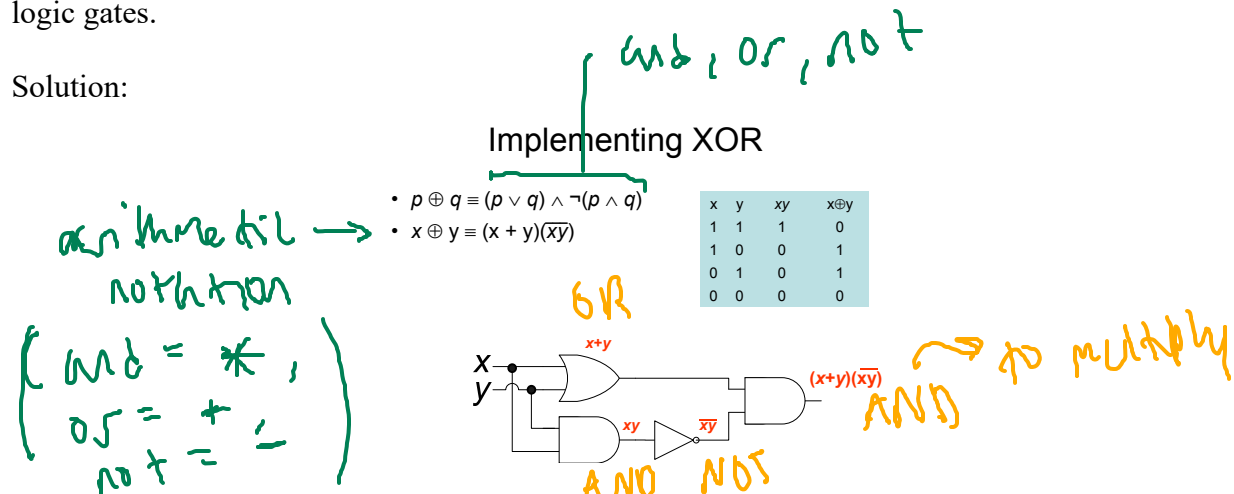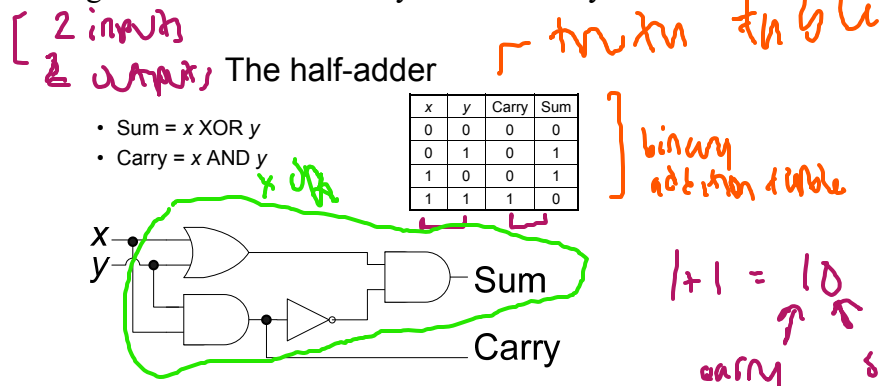**3. Half-Adder:** The following circuit sums two binary bits with carry.Exercise: Build a circuit to compute the Boolean expression $(x + \bar{y} \cdot (x + \bar{z}))z$.